

Lecture 16: Basic CPU Design

- Today's topics:
 - Single-cycle CPU
 - Multi-cycle CPU


Basic MIPS Architecture

- Now that we understand clocks and storage of states, we'll design a simple CPU that executes:
 - basic math (add, sub, and, or, slt)
 - memory access (lw and sw)
 - branch and jump instructions (beq and j)

Implementation Overview

- We need memory
 - to store instructions
 - to store data
 - for now, let's make them separate units
- We need registers, ALU, and a whole lot of control logic
- CPU operations common to all instructions:
 - use the program counter (PC) to pull instruction out of instruction memory
 - read register values

View from 30,000 Feet

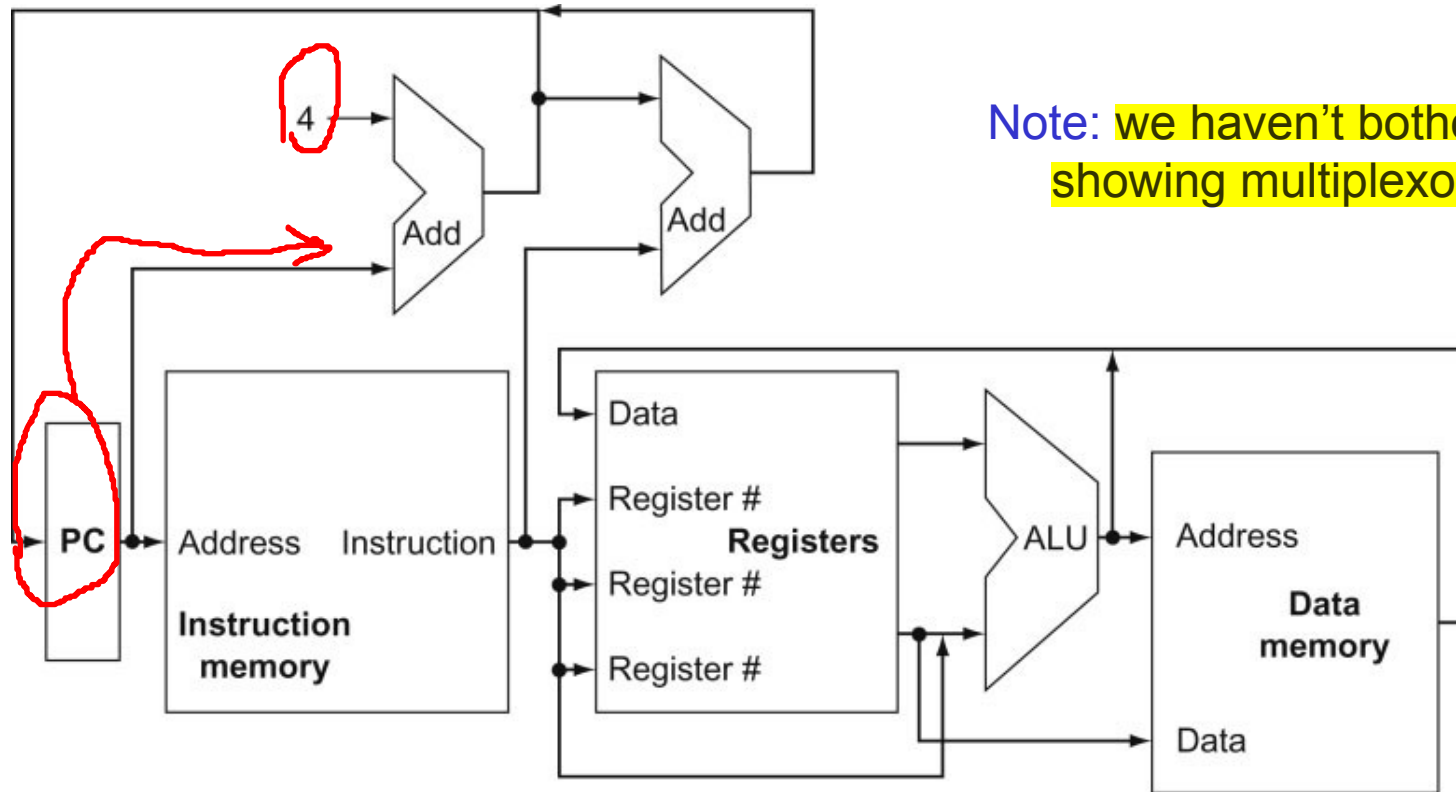

Note: we haven't bothered showing multiplexors

- What is the role of the Add units? ไว้เพิ่ม PC กับ Jump
- Explain the inputs to the data memory unit ไว้ใช้ตำแหน่ง Address ที่จะเก็บ
- Explain the inputs to the ALU ใ้รับคำสั่งคำนวณ
- Explain the inputs to the register unit 3 Register ไว้เขียน 1 Data ไว้ Load

Source: H&P textbook




- ที่ซึ่งก็มี clock ไว้ latch ข้อมูล

5

5

Implementing R-type Instructions

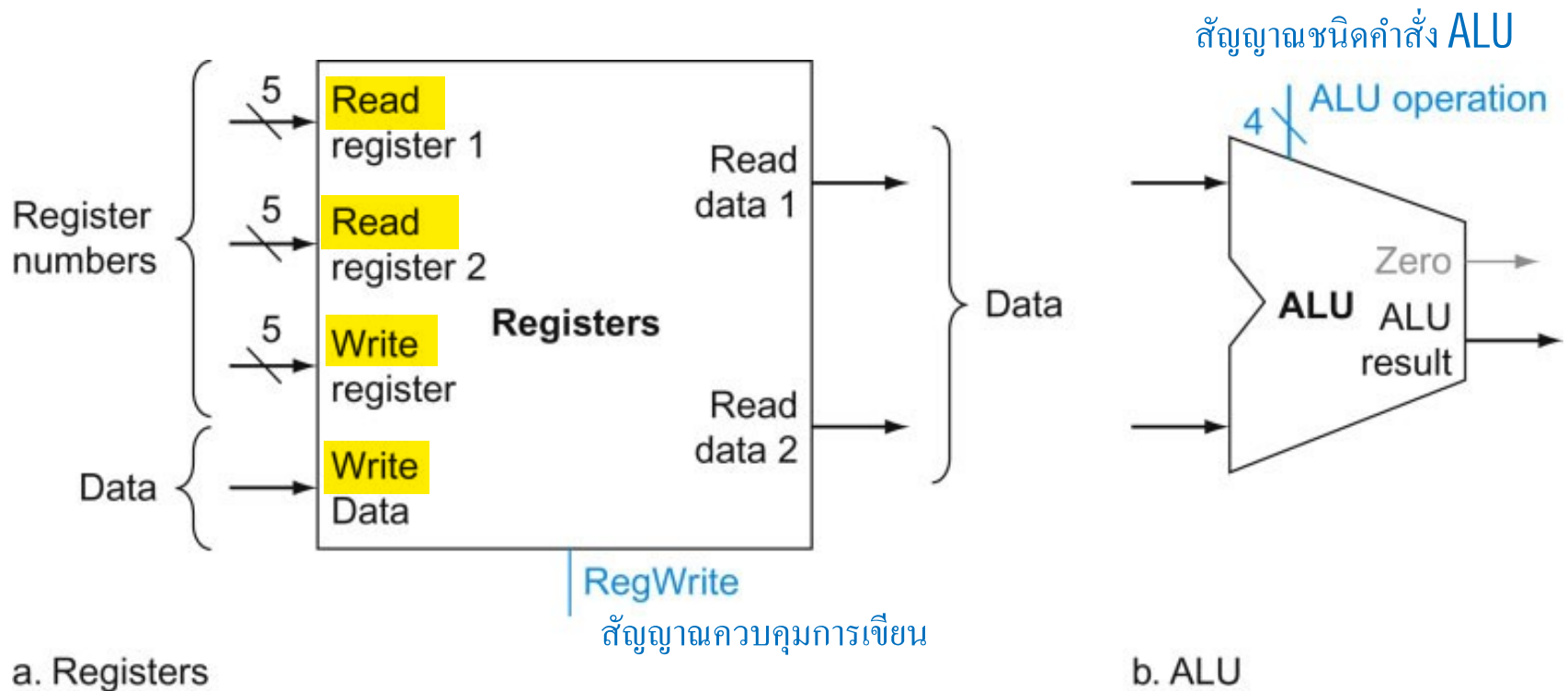
- Instructions of the form `add $t1, $t2, $t3`
- Explain the role of each signal



Source: H&P textbook

Implementing Loads/Stores

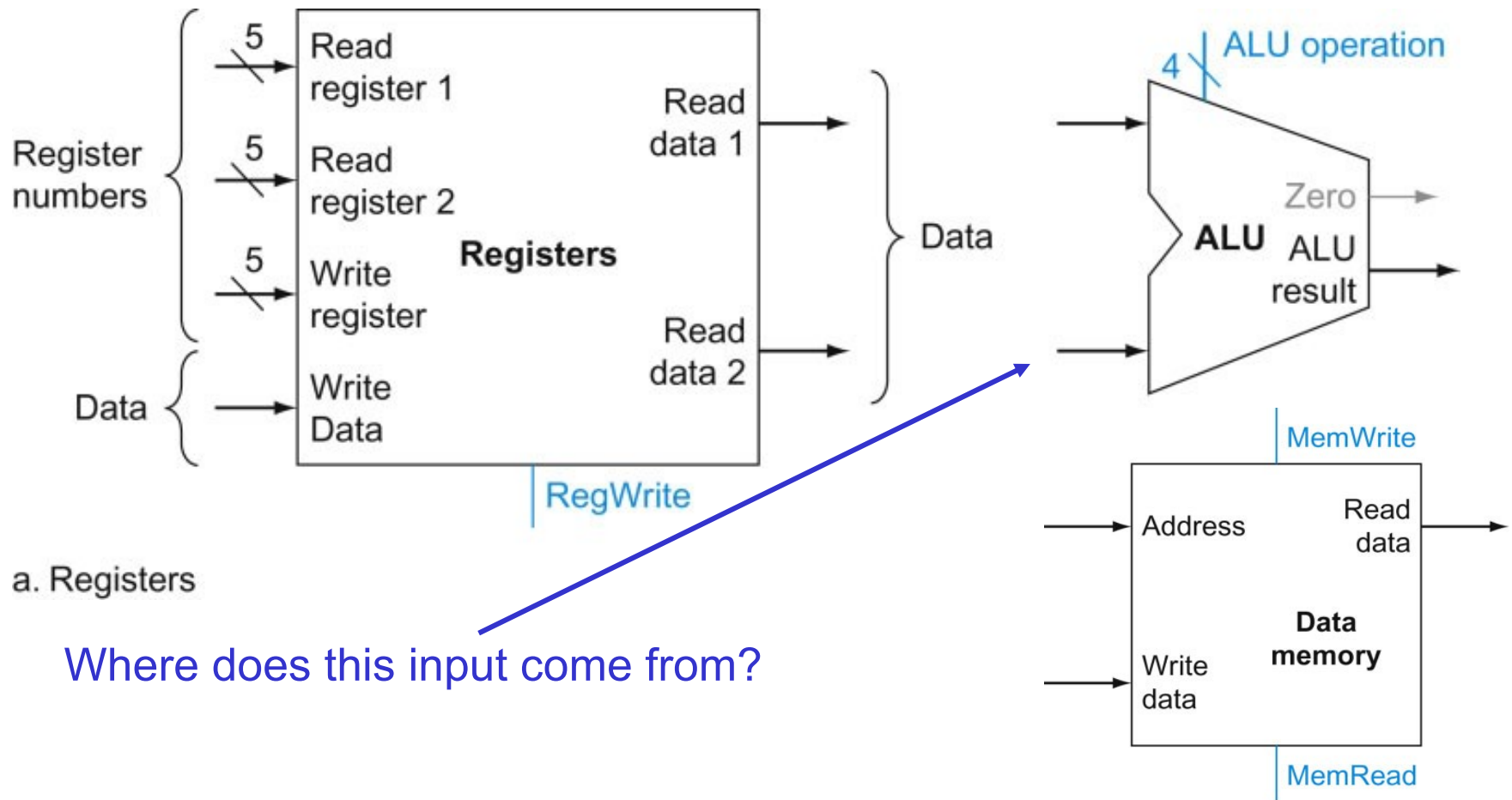
- Instructions of the form `lw $t1, 8($t2)` and `sw $t1, 8($t2)`



Where does this input come from?


Implementing J-type Instructions

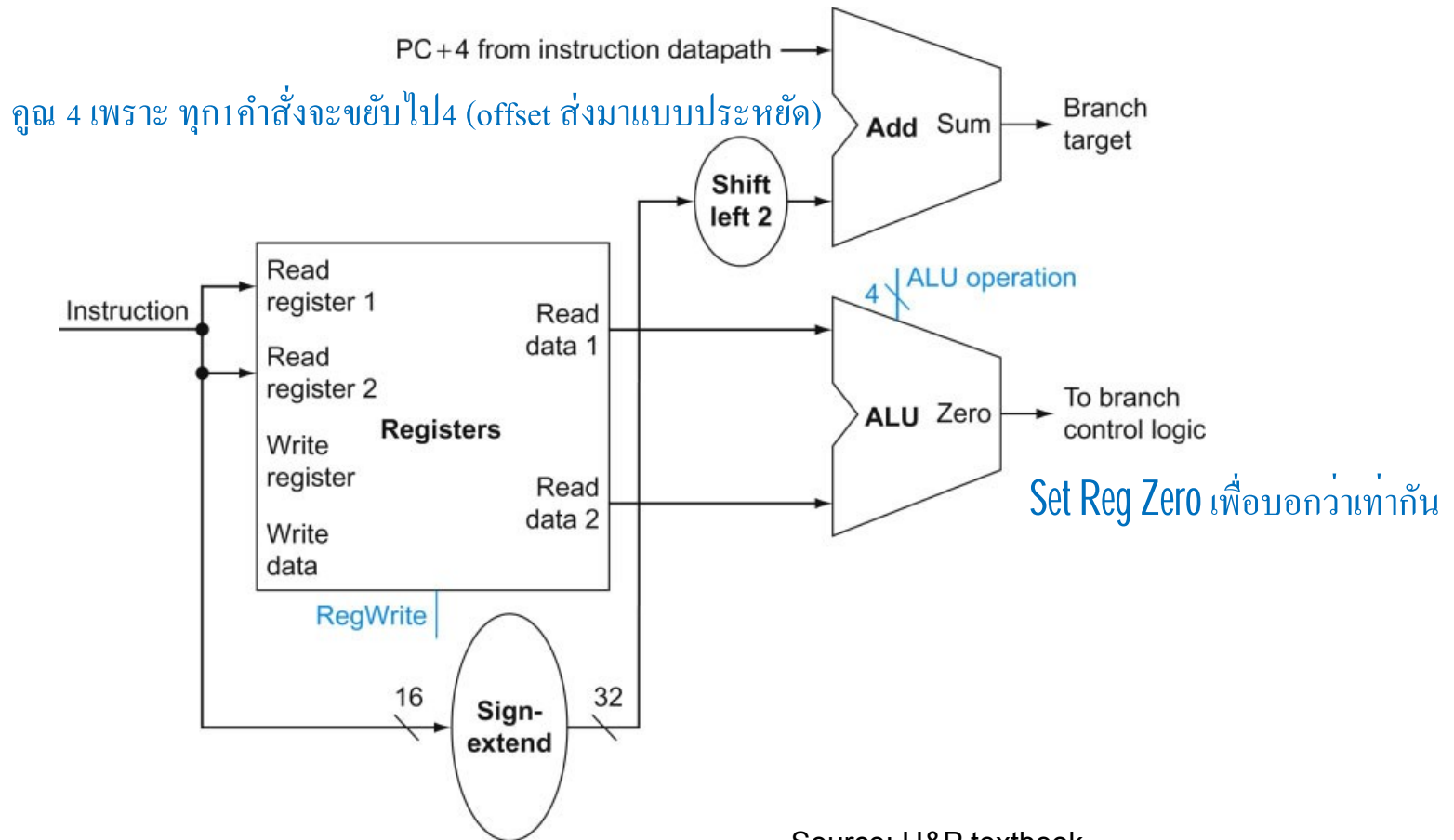- Instructions of the form `beq $t1, $t2, offset`




Source: H&P textbook
offset มัน 16 บิต แต่ Add รับ 32 บิต เลขขยาย โดยเอา MSB เข้าไปจนครบ 32

View from 10,000 Feet

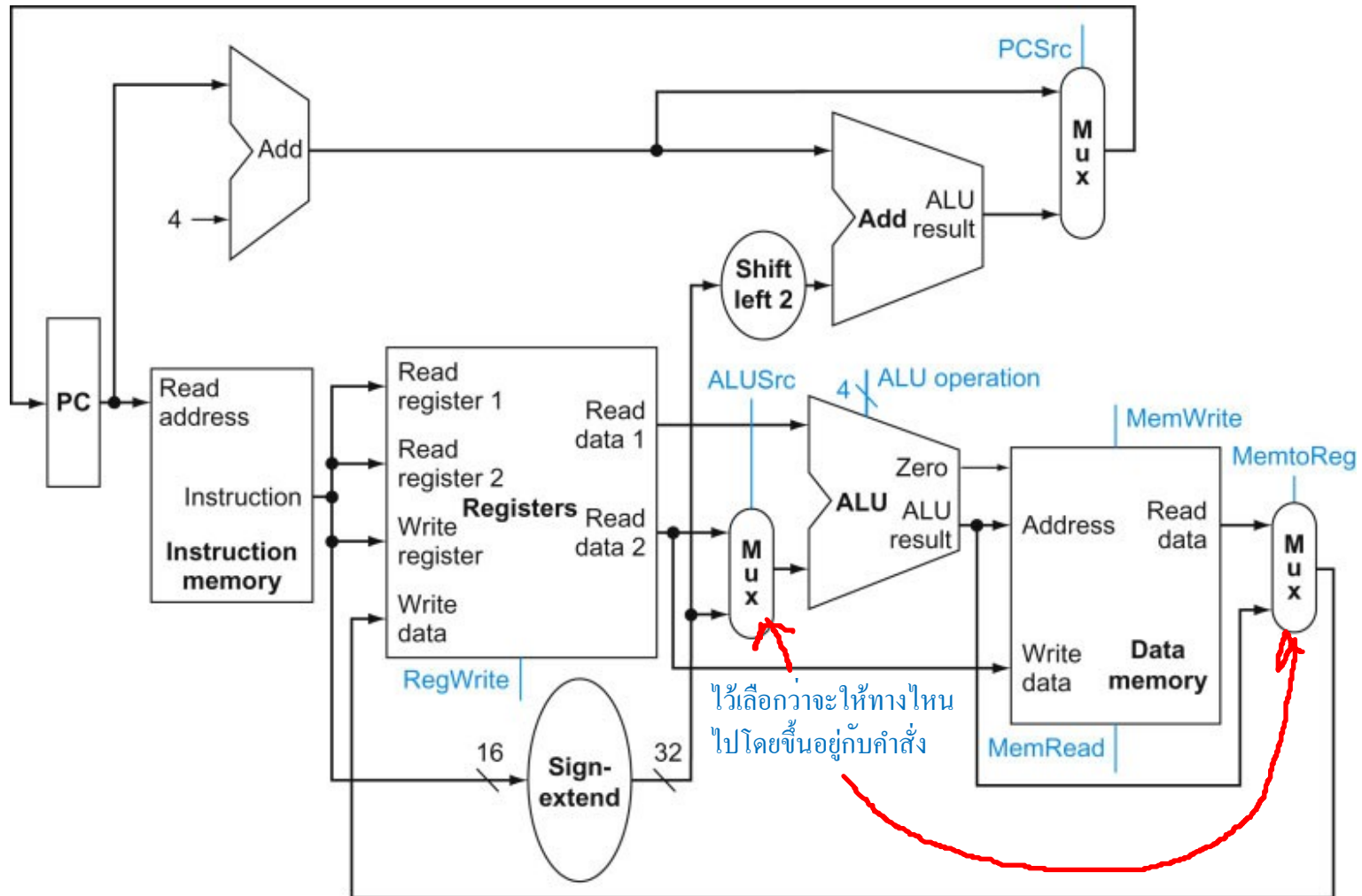


View from 5,000 Feet

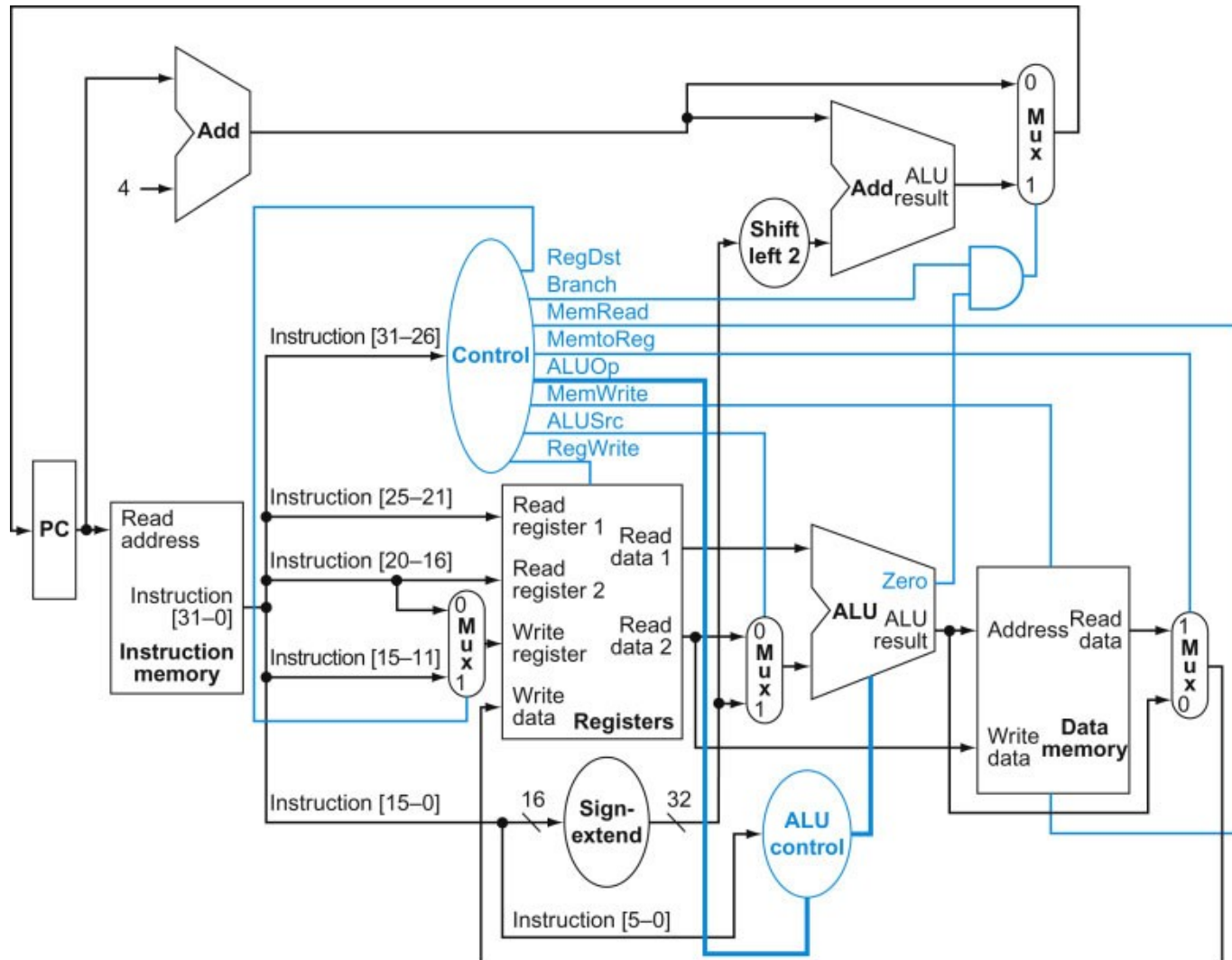

Latches and Clocks in a Single-Cycle Design

ทั้งหมดนี้รันในหนึ่ง cycle

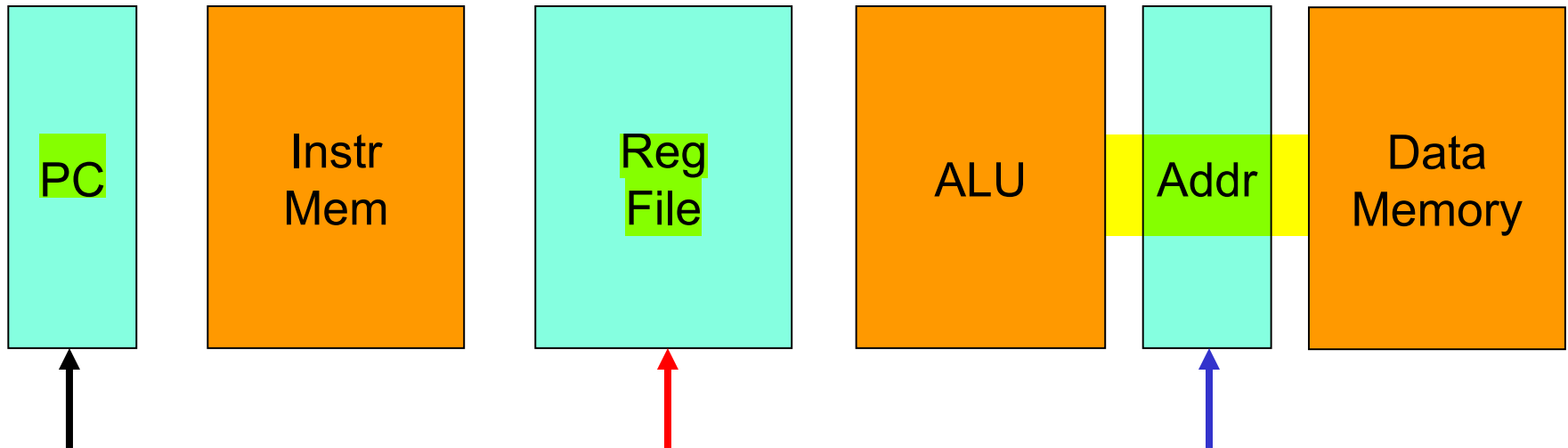

- The entire instruction executes in a single cycle
- Green blocks are latches
- At the rising edge, a new PC is recorded
- At the rising edge, the result of the previous cycle is recorded
- At the falling edge, the address of LW/SW is recorded so we can access the data memory in the 2nd half of the cycle

Multi-Stage Circuit

- Instead of executing the entire instruction in a single cycle (a single stage), let's break up the execution into multiple stages, each separated by a latch

